
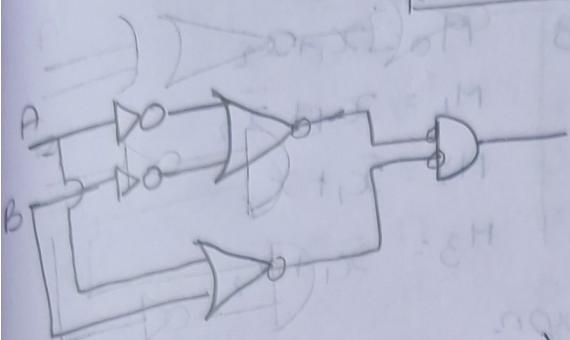


XOR using NOR gate

$$(\text{XOR} = \bar{A}B + A\bar{B})$$

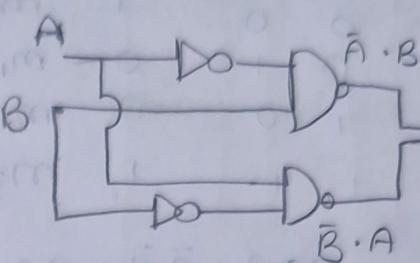

XOR using NAND gate



(minterm & maxterm) synthesis :-

ROW NO	x_1	x_2	minterm	maxterm
0	0	0	$m_0 = \bar{x}_1 \cdot \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 \cdot x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \cdot \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 \cdot x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

y	A	B	$A \oplus B$
1	0	0	0
1	0	1	1
0	1	0	1
1	1	1	0

$$A \oplus B = \bar{A}B + A\bar{B} \Rightarrow \text{SOP expn.}$$

$$y = m_0 + m_1 + m_3 = \sum m(0, 1, 3) \rightarrow \text{(minterm list)}$$

$$= \bar{A}\bar{B} + \bar{A}B + A\bar{B}$$

↓
canonical SOP expⁿ

$$m_0 = \bar{A} + \bar{B} + B(A + \bar{A})$$

$$m_1 = \bar{A} \cdot \bar{B} + B \cdot \bar{B} \rightarrow \bar{A} + B \cdot \bar{B}$$

[canonical \rightarrow each product term is a minterm]

$$(A + \bar{B})(\bar{A} + B) = 1$$

$$\bar{A} \cdot \bar{B} + \bar{A} \cdot B + A \cdot \bar{B} + A \cdot B = 1$$

XNOR gate

A	B	$A \oplus B = \overline{A \oplus B}$	maxterm
0	0	$m_0 = \bar{A}\bar{B} + A\bar{B}$	$M_0 = x_1 + x_2$
0	1	$m_1 = \bar{A}B$	$M_1 = x_1 + \bar{x}_2$
1	0	$m_2 = A\bar{B}$	$M_2 = \bar{x}_1 + x_2$
1	1	$m_3 = AB$	$M_3 = \bar{x}_1 + \bar{x}_2$

$$AOB = \bar{A}\bar{B} + AB \rightarrow SOP \text{ exprn}$$

ex. $Y = m_0 + m_3$. (compliment)

R.no:	x_1	x_2	x_3	minterm	O/P Z	Z'	maxterm
0	0	0	0	$m_0 = \bar{A}\bar{B}\bar{C}$	0	1	$M_0 = \bar{m}_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{A}\bar{B}C$	1	0	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{A}BC$	0	1	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{A}BC$	0	1	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = A\bar{B}\bar{C}$	1	0	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = A\bar{B}C$	1	0	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = AB\bar{C}$	0	1	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = ABC$	1	0	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$Z(x_1, x_2, x_3) = m_1 + m_3 + m_4 + m_7$$

MSB LSB
 (most significant bit) $= \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1\bar{x}_2\bar{x}_3 + x_1x_2x_3$

(canonical SOP exprⁿ)

$$= \sum m(1, 3, 4, 7).$$

Problem stat: Th \Rightarrow whenever we press a even number then the bulb should glow. (with 3 input)
write logical expⁿ.

→ minterm list for compliment;

canonical SOP expⁿ

$$Z' = \sum m(0, 2, 5, 6)$$

$$= \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1x_2\bar{x}_3 + x_1\bar{x}_2x_3 + \bar{x}_1\bar{x}_2\bar{x}_3$$

$$= \bar{x}_1\bar{x}_3(x_2 + \bar{x}_2) + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

(P.O)

R.NO	A	B	C	Z	
0	0	0	0	1	$-(\bar{x}_1 + x_2)\bar{x}_3 + x_1\bar{x}_2x_3$
1	0	0	1	0	$= \bar{x}_1\bar{x}_3 + x_2\bar{x}_3 + x_1\bar{x}_2x_3$
2	0	1	0	1	
3	0	1	1	0	↓ minimized SOP exp?
4	1	0	0	1	
5	1	0	1	0	
6	1	1	0	1	
7	1	1	1	0	


$$Z(A, B, C) = m_0 + m_2 + m_4 + m_6.$$

$$(m_0 = \bar{m}(0, 2, 4, 6)).$$

$$\therefore \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C}.$$

$$= \bar{A}\bar{C}(B + \bar{B}) + A\bar{C}(B + \bar{B})$$
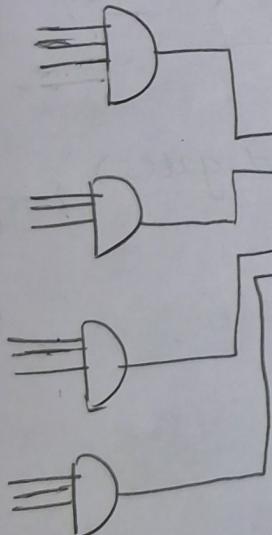
$$= \bar{A}\bar{C} + A\bar{C} = \bar{C}.$$




cost: no. of gates at input

$$= 16 + 5 \Rightarrow 21$$

cost of reduced one $\Rightarrow 0$

neat way:

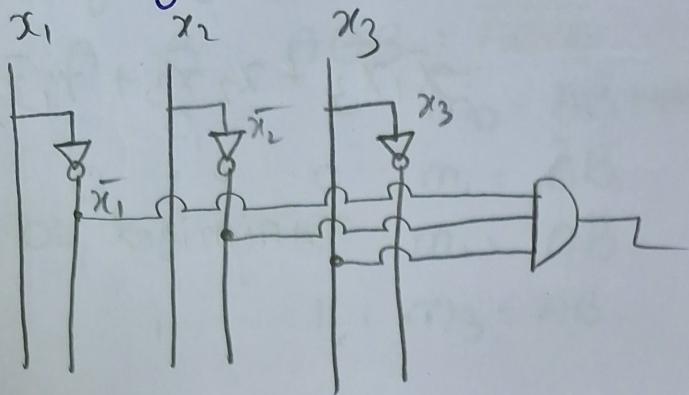


* when we implement SOP exprn using minterms,
we get two level circuit.

first level \rightarrow AND gates


and second level \rightarrow one OR gate

[this is called ANDOR combination]

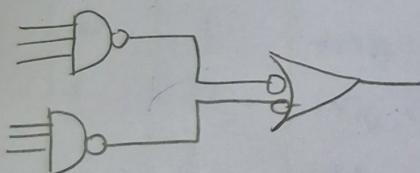This combination can be easily converted to
NAND-NAND gates.



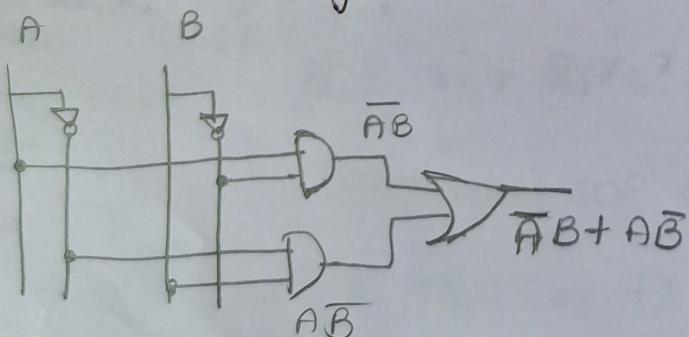Draw XOR using NAND gates: (4/5 nand gates)



Draw XNOR using NAND:

minterm:

It is a product term in which all the input variables are there in true or complemented form.

maxterm:

It is a sum term in which all the input variables are there in true/complemented form.


$$\rightarrow M_0 = \bar{m}_0$$

(whichever the o/p is zero).


$$A \oplus B = \sum_m (1, 2) = [M_0 \cdot M_3 = (x_1 + x_2) \cdot (\bar{x}_1 + \bar{x}_2)]$$

$$\Rightarrow \prod_M (0, 3)$$

→ logic diagram for POS:-

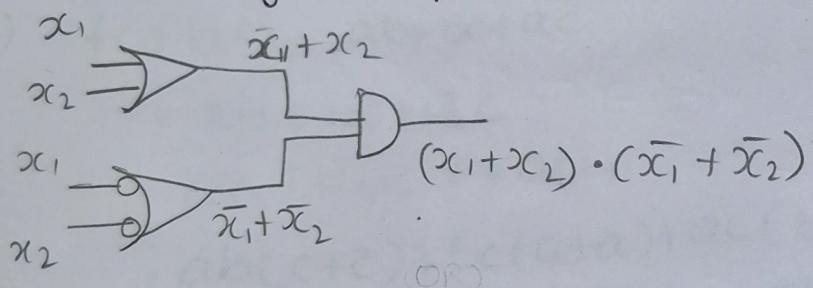


using universal gates (NOR)

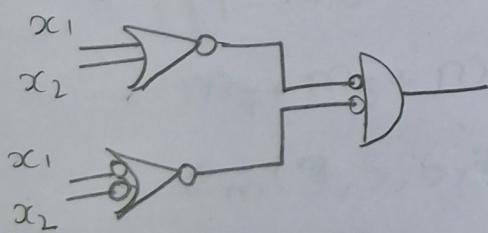


→ Implement maxterm using xNOR gate:-

$$z(x_1, x_2) = \cancel{\prod_M (1, 2)} = M_1 \cdot M_2$$
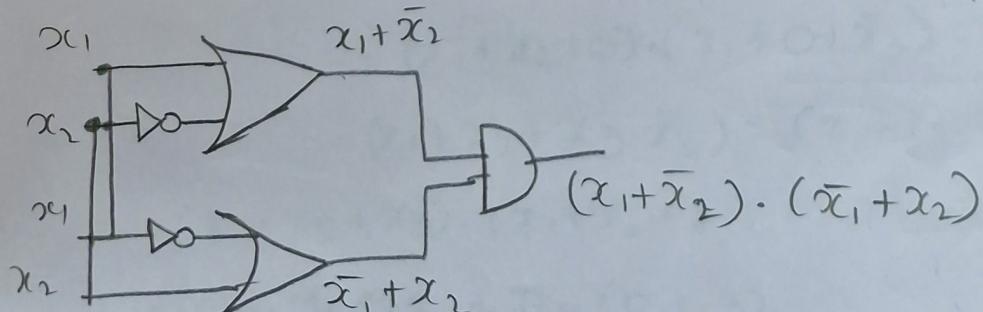
$$x_1 \odot x_2 = (x_1 + \bar{x}_2) \cdot (\bar{x}_1 + x_2)$$



using NOR:

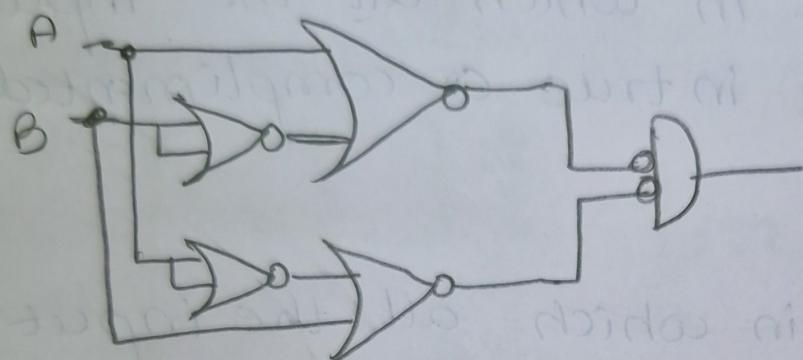

For 3 input;

$$f(x_1, x_2, x_3) = \Sigma_m(1, 3, 4, 7)$$

$$(x_1 + x_2 + x_3) = \prod_M(0, 2, 5, 6)$$

$$\Rightarrow (x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + x_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3) \cdot (\bar{x}_1 + \bar{x}_2 + x_3)$$

$$(x_1 + x_2 + x_3) \cdot \prod_M(0, 2, 5, 6)$$

\therefore sum of minterms

$$(x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + x_3)$$

$$(x_1 + x_2 + x_3) \cdot (x_1 + \bar{x}_2 + x_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3) \cdot (\bar{x}_1 + \bar{x}_2 + x_3)$$



write minterm & for maxterm (minterm - all 3 inputs should be there)

- $$f(x_1, x_2, x_3) = x_1 + x_2 \bar{x}_3$$

$$= x_1 \cdot 1 + 1 \cdot x_2 \bar{x}_3$$

$$\Rightarrow x_1 \cdot (x_2 + \bar{x}_2) + (x_1 + \bar{x}_1) \cdot x_2 \cdot \bar{x}_3$$

$$= x_1 x_2 \cdot 1 + x_1 \bar{x}_2 \cdot 1 + x_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 \bar{x}_3$$

$$= x_1 x_2 (x_3 + \bar{x}_3) + x_1 \bar{x}_2 (x_3 + \bar{x}_3) + x_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 \bar{x}_3$$

$$= x_1 x_2 x_3 + x_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 + \bar{x}_1 x_2 \bar{x}_3$$

$$= m_7 + m_6 + m_5 + m_4 + m_2$$

↓ canonical sop exp

$$= \sum_m (2, 4, 5, 6, 7).$$

maxterm, $\prod_M (0, 1, 3, 8)$.

- $$f(a, b, c) = ab + bc + ac$$

$$= ab + bc + ac$$

$$= ab \cdot 1 + bc \cdot 1 + ac \cdot 1$$

$$= ab(c + \bar{c}) + bc(a + \bar{a}) + ac(b + \bar{b})$$

$$= abc + a\bar{b}c + \bar{a}bc + abc + a\bar{b}c$$

$$= m_7 + m_6 + m_3 + m_5$$

$$= \sum_m (3, 5, 6, 7)$$

maxterm, $\prod_M (0, 1, 2, 4)$

(1) DO in POS form

$$f(x_1, x_2, x_3) = x_1 + x_2 \cdot \bar{x}_3$$

$$= (x_1 + x_2) \cdot (x_1 + \bar{x}_3)$$

$$= (x_1 + x_2 + 0) \cdot (x_1 + 0 + \bar{x}_3)$$

$$= (x_1 + x_2 + x_3 \cdot \bar{x}_3) \cdot (x_1 + x_2 \cdot \bar{x}_2 + \bar{x}_3)$$

$$= (x_1 + x_2 + x_3) \cdot (x_1 + x_2 + \bar{x}_3) \cdot (x_1 + x_2 + \bar{x}_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3)$$

$$= M_0 \cdot M_1 \cdot M_3 = \prod_M (0, 1, 3).$$

4) Write func. f in which 3 input variables there when $f=1$, majority of inputs are 1.

	x_1	x_2	x_3	f
0	0	0	0	$\bar{x}_1 \cdot \bar{x}_2 \cdot \bar{x}_3 + 1 \cdot 1 \cdot 1$
1	0	0	0	$(\bar{x}_1 + x_1) \cdot (\bar{x}_2 + x_2) \cdot (\bar{x}_3 + x_3)$
2	0	0	1	$\bar{x}_1 \cdot \bar{x}_2 \cdot x_3 + (\bar{x}_1 + x_1) \cdot (\bar{x}_2 + x_2) \cdot 1$
3	0	1	0	$\bar{x}_1 \cdot x_2 \cdot \bar{x}_3 + 0 \cdot x_2 \cdot x_3 + 1 \cdot \bar{x}_2 \cdot 1 \cdot x_3$
4	0	1	1	$(\bar{x}_1 + x_1) \cdot x_2 \cdot x_3 + (\bar{x}_1 + x_1) \cdot (\bar{x}_2 + x_2) \cdot x_3$
5	1	0	0	$x_1 \cdot \bar{x}_2 \cdot \bar{x}_3 + (\bar{x}_1 + x_1) \cdot (\bar{x}_2 + x_2) \cdot (\bar{x}_3 + x_3)$
6	1	0	1	$x_1 \cdot \bar{x}_2 \cdot x_3 + (\bar{x}_1 + x_1) \cdot (\bar{x}_2 + x_2) \cdot 1$
7	1	1	1	$x_1 \cdot x_2 \cdot x_3 + 1 \cdot 1 \cdot 1$

$$\therefore f = m_3 + m_5 + m_6 + m_7$$

$$= \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3$$

$$= x_1 x_2 (x_3 + \bar{x}_3) + \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3$$

$$= x_1 x_2 + \bar{x}_1 x_2 x_3 + x_1 \bar{x}_2 x_3$$

$$= \bar{x}_1 x_2 x_3 + x_1 (\bar{x}_2 x_3 + x_2)$$

$$= \bar{x}_1 x_2 x_3 + x_1 (x_2 + x_3)$$

$$= \bar{x}_1 x_2 x_3 + x_1 x_2 + x_1 x_3$$

$$= x_2 (\bar{x}_1 x_3 + x_1) + x_1 x_3$$

$$= x_2 (x_1 + x_3) + x_1 x_3$$

$$= x_1 x_2 + x_2 x_3 + x_1 x_3$$



OR

COST - 4 + 9



= 13

Q) A circuit that controls a digital system has 3 inputs (x_1, x_2, x_3). It has to recognise 3 diff conditions.


Condition 'A' is true if x_3 is T & either x_1 is T or x_2 is F.

Cond. 'B' is T if x_1 is T & either x_2 or x_3 is F.

Cond. 'C' is T if x_2 is T & either x_1 is T or x_3 is F.

The control circuit must produce 1, if atleast two of conditions A, B, C is true. Design a circuit.

x_1	x_2	x_3	$A = x_3 \cdot (x_1 + \bar{x}_2)$	$B = x_1 \cdot (\bar{x}_2 + \bar{x}_3)$	$C = x_2 \cdot (x_1 + \bar{x}_3)$
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

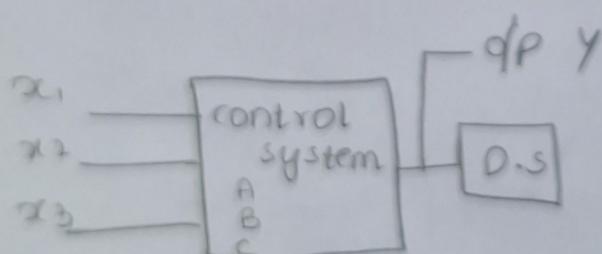

$$A = x_3 \cdot (x_1 + \bar{x}_2)$$

$$B = x_1 \cdot (\bar{x}_2 + \bar{x}_3)$$

$$C = x_2 \cdot (x_1 + \bar{x}_3)$$

$$Y = A \cdot B + B \cdot C + A \cdot C + A \cdot B \cdot C$$

$$= AB + BC + AC (1 + B)$$

$$= AB + BC + AC$$

$$= x_3 \cdot (x_1 + \bar{x}_2) x_1 \cdot (\bar{x}_2 + \bar{x}_3) + x_1 (\bar{x}_2 + \bar{x}_3) \cdot x_2 (x_1 + \bar{x}_3)$$

$$+ x_3 x_2 (x_1 + \bar{x}_2) (x_1 + \bar{x}_3)$$

$$= x_1 x_3 + x_1 \bar{x}_2 x_3 (\bar{x}_2 + \bar{x}_3) + x_1 (0) + x_1 x_2 \bar{x}_3 (x_1 + \bar{x}_3)$$
$$+ x_1 x_2 x_3 + 0 (x_1 + \bar{x}_3)$$

$$= x_1 x_3 + x_1 \bar{x}_2 x_3 + 0 + x_1 x_2 \bar{x}_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3$$

$$= x_1 x_3 + x_1 x_2 \bar{x}_3 + x_1 x_2 x_3.$$

$$\Rightarrow x_1 x_2 (x_3 + \bar{x}_3) + x_1 x_3$$

$$= x_1 x_2 + x_1 x_3.$$

$$\Rightarrow x_1 (x_2 + x_3)$$