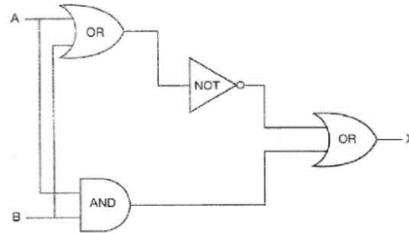


## Digital Electronics (Tutorial 1)

- Write Boolean Expression for the following circuit. Draw the Timing diagram for inputs A and B(10,11,01,10,00)



- Use algebraic transformations to prove or disprove that the two circuits given in Fig.1 implement the same function(do not use truth table or kmap)

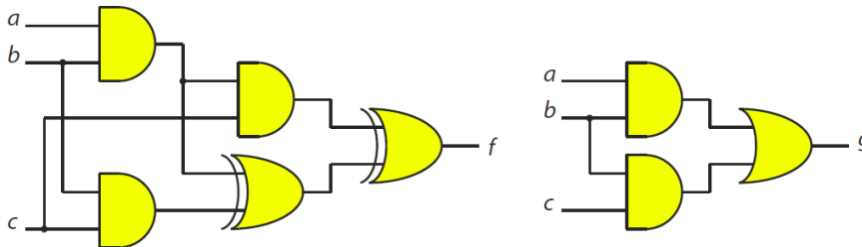


Fig. 1

- Write Truth table for both circuits and verify their equality.
- Draw logic diagrams to implement the following Boolean expressions:
  - $f = [(u + x') (y' + z)]$
  - $f = (u \oplus y)' + x$
  - $f = (u' + x') (y + z')$
- Truthtable of output Y for inputs A, B and C are given.

A	0	1	0	1	0	1	0	1
B	0	0	1	1	0	0	1	1
C	0	0	0	0	1	1	1	1
Y	1	1	1	0	1	0	0	0

- Write Minterm list corresponding to output Y
- Write Maxterm list corresponding to output Y
- Write Canonical SOP expression for Y
- Write Canonical POS expression for Y
- Reduce expression obtained from (iii) and draw circuit diagram
- Reduce expression obtained from (iv) and draw circuit diagram
- Compare the cost of ckt diagram from (v) and (vi)

Q 6.

Simplify the following Boolean functions  $T_1$  and  $T_2$  to a minimum number of literals:

<b>A</b>	<b>B</b>	<b>C</b>	<b>T<sub>1</sub></b>	<b>T<sub>2</sub></b>
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

Q 7.

Simplify the following Boolean expressions to a minimum number of literals:

(a)\*  $ABC + A'B + ABC'$

(b)\*  $x'yz + xz$

(c)\*  $(x + y)'(x' + y')$

(d)\*  $xy + x(wz + wz')$

(e)\*  $(BC' + A'D)(AB' + CD')$

(f)  $(a' + c')(a + b' + c')$